- 1. Remove both ICs and connect power
- 2. Print out the component overlay to mark off the test results
- 3. Perform all the voltage tests in the assembly guide
  - a. this confirms the following are working OK and you can check them off on the component overlay sheet: SV1, C2, C4, C6, C3, C5
  - b. remove all jumpers, inputs and outputs
- 4. Plug signal from a VCO into DCIN Jack A
  - a. using a breadboard jumper and alligator clips to a jack plug, connect pin 4 of IC1 socket to your output (mixer etc.)
  - b. you should faintly hear the output from the vco; you may have to increase the volume on your output
  - c. disconnect the output to the audio
  - d. run a 5V DC voltage into the DCIN Jack A
  - e. measure the voltge at pin 4 of IC1 open socket. You should get approximately 9 or 10mV
  - f. this confirms the following are working OK and you can check them off on the component overlay sheet: J1, R3, R5
  - g. remove all jumpers, inputs and outputs
- 5. Plug signal from a VCO into DCIN Jack B
  - a. using a breadboard jumper and alligator clips to a jack plug, connect pin 13 of IC1 socket to your output (mixer etc)
  - b. you should faintly hear the output from the vco; you may have to increase the volume on your output
  - c. disconnect the output to the audio
  - d. run a 5V DC voltage into the DCIN Jack B
  - e. measure the voltge at pin 13 of IC1 open socket,. You should get approximately 9 or 10mV
  - f. this confirms the following are working OK and you can check them off on the component overlay sheet: J8, R20, R15
  - g. remove all jumpers, inputs and outputs

- 6. Measure the voltage at pin 3 of IC1 open socket
  - a. adjust R1 trimmer from 0 fully CCW to fully CW
  - b. you should see the voltage move from approx -2.5mV to +2.6mV
  - c. this confirms the following are working OK and you can check them off on the component overlay sheet: R1, R2, R4
- 7. Measure the voltage at pin 14 of IC1 open socket
  - a. adjust R14 trimmer from 0 fully CCW to fully CW
  - b. you should see the voltage move from approx -2.5mV to +2.6mV
  - c. this confirms the following are working OK and you can check them off on the component overlay sheet: R14, R23, R16
- 8. Measure the voltage at pin 2 of IC2 open socket
  - a. adjust VR1 from fully CW to fully CCW
  - b. you should see the voltage move from between approx 0V to +6.5V, depending on the value you selected for R10
  - c. this confirms the following are working OK and you can check them off on the component overlay sheet: VR1, R10, R11
- 9. Measure the voltage at pin 9 of IC2 open socket
  - a. adjust VR2 from fully CW to fully CCW
  - b. you should see the voltage move from approx 0V to +6.5V, depending on the value you selected for R26
  - c. this confirms the following are working OK and you can check them off on the component overlay sheet: VR2, R26, R25
- 10. Run a 5V DC voltage into a CV Jack A
  - a. measure the voltge at pin 2 of IC2 open socket
  - b. adjust VR1 to 0
  - c. you should measure between +1 and +2V, depending on the value you selected for R10
  - d. repeat for the other CV Jack A
  - e. this confirms the following are working OK and you can check them off on the component overlay sheet: J3, J4, R8, R9
  - f. remove all jumpers, inputs and outputs

- 11. Run a 5V DC voltage into a CV Jack B
  - a. measure the voltge at pin 9 of IC2 open socket
  - b. adjust VR2 to 0
  - c. you should measure between +1 and +2V, depending on the value you selected for R26
  - d. repeat for the other CV Jack B
  - e. this confirms the following are working OK and you can check them off on the component overlay sheet: J9, J10, R21, R22
  - f. remove all jumpers, inputs and outputs

### 12. Reinstall IC2 (TL074) but not IC1

- 13. Measure the voltage at pin 1 of IC1 open socket
  - a. adjust VR1 from fully CCW to fully CW
  - b. you should see the voltage move from between approx 0V to -10V as you rotate the pot
  - c. this confirms the following are working OK and you can check them off on the component overlay sheet: D1, R13, R12, Q1, IC2 (partly)
- 14. Measure the voltage at pin 16 of IC1 open socket
  - a. adjust VR2 from fully CCW to fully CW
  - b. you should see the voltage move from between approx 0V to -10V as you rotate the pot
  - c. this confirms the following are working OK and you can check them off on the component overlay sheet: D2, R24, R18, Q2, IC2 (partly)
- 15. Using a breadboard jumper, short pins 4 and 5 of IC1 open socket
  - a. connect OUTA socket to your output (mixer etc)
  - b. plug signal from a VCO into DCIN Jack A
  - c. you should hear the output from the VCO
  - d. plug signal from a VCO into ACIN Jack A
  - e. you should hear the output from the VCO
  - f. this confirms the following are working OK and you can check them off on the component overlay sheet: C8, R6, R7, IC2 (partly), J5, J2, C1
  - g. remove all jumpers, inputs and outputs

- 16. Using a breadboard jumper, short pins 12 and 13 of IC1 open socket
  - a. connect OUTB socket to your output (mixer etc)
  - b. plug signal from a VCO into DCIN Jack B
  - c. you should hear the output from the VCO
  - d. plug signal from a VCO into ACIN Jack B
  - e. you should hear the output from the VCO
  - f. this confirms the following are working OK and you can check them off on the component overlay sheet: C9, R19, R17, IC2 (partly), J6, J8, C12
  - g. remove all jumpers, inputs and outputs
- 17. Install a different IC1 if all the above tests pass